






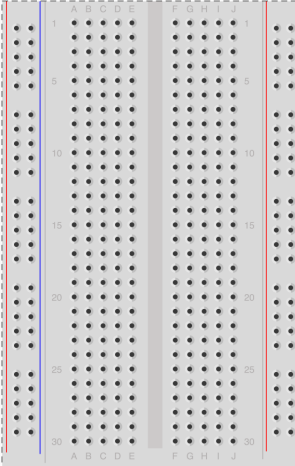 

 






# Build Your Own Cicada Sensor Kit


These instructions also live at: [wny.cc/bugkit](http://wny.cc/bugkit)

## Parts List

- |  |  |  |
|--|--|--|
|  <p><b>Microcontroller</b><br/>ATmega328P<br/>1x</p> <p>Pre-programmed<br/>by Radiolab</p> |  <p><b>Capacitor</b><br/>10uF / 10V<br/>1x</p>    |  <p><b>Breadboard</b><br/>1x</p>   |
|  |  <p><b>Capacitor</b><br/>100nF / 6.3V<br/>1x</p>  |  |
|  <p><b>LEDs</b><br/>9x</p>   |  <p><b>Capacitors</b><br/>100nF / 6.3V<br/>2x</p> |  |
|  <p><b>Thermistor</b><br/>1x</p>   |  <p><b>Orange wires</b><br/>3 inches<br/>4x</p>   |  |
|  <p><b>Resistor</b><br/>47k ohm, 0.1%<br/>1x</p>   |  <p><b>Green wires</b><br/>5 inches<br/>10x</p>   |  |
|  <p><b>Resistors</b><br/>220 ohm<br/>9x</p>  |  <p><b>Long wires</b><br/>12 inches<br/>2x</p>    |  <p><b>2 AA Battery Holder</b><br/>1x</p> <p><b>1.5V AA Batteries</b><br/>2x</p> |

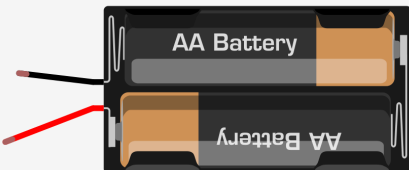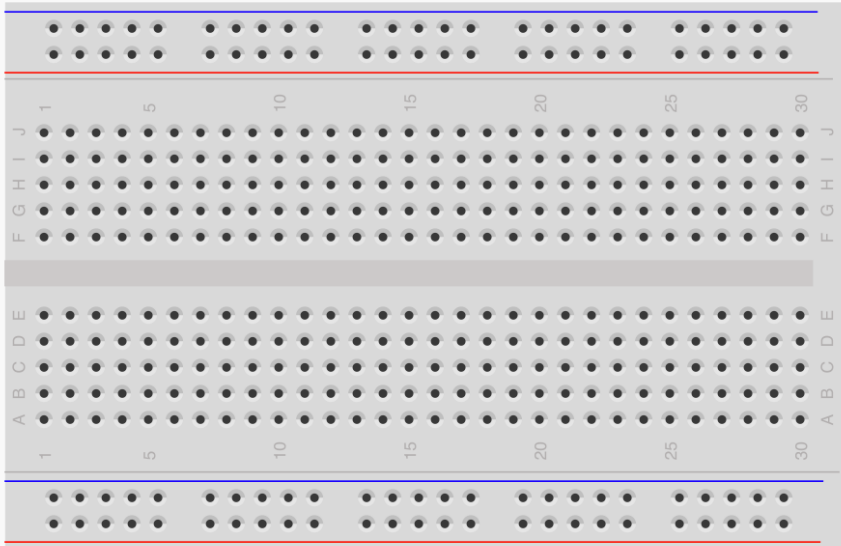

You have your breadboard...

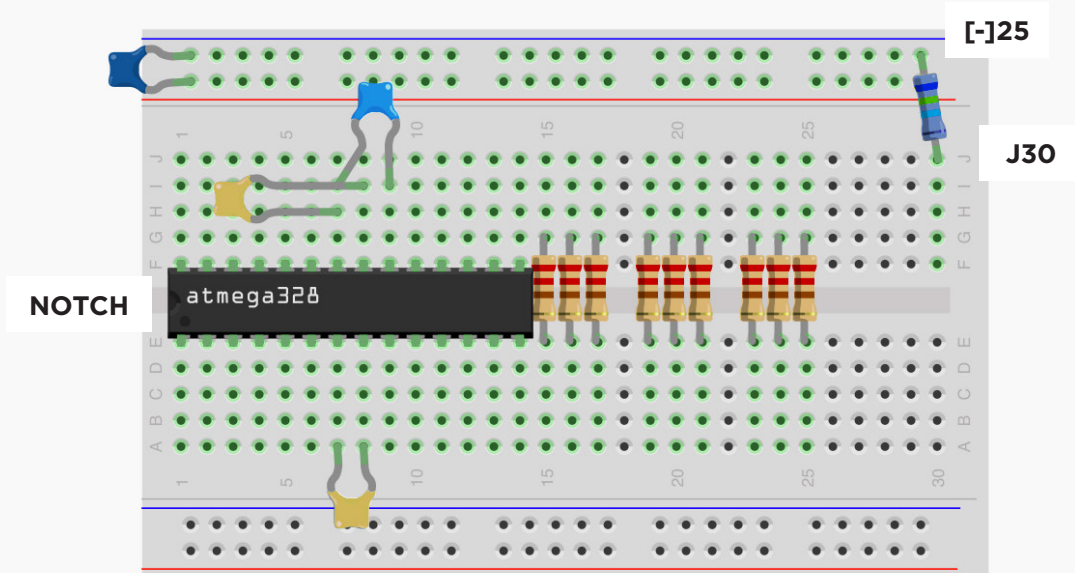

...and then you put your parts on it.

220 ohm resistors go from

**E15 to G15**

**E16 to G16**

**E17 to G17**

**E19 to G19**

**E20 to G20**

**E21 to G21**

**E23 to G23**

**E24 to G24**

**E25 to G25**

Microcontroller goes on the left of the breadboard, from **E/F1** to **E/F 14**. The notched side points towards the end.

The 47k ohm resistor goes from **[-]25** to **J30**.

Dark blue capacitor goes in **[+]1** and **[-]1**.

Light blue capacitor goes in **i7** and **i9**.

Tan capacitors goes in **H7** and **I8**, **A7** and **A8**.

# The Adam DePrince Splice

(named after our developer, Adam DePrince)

Set aside the breadboard for a minute. Do up your thermistor by attaching the blue wires to its ends.

**1** Take one end of the thermistor and one end of the blue wire.




**2** You want to make a bend in the end of the blue wire...



**3** ...and coil the end of the thermistor around that bend.



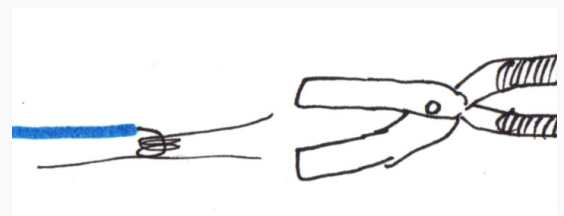**4** Then, use a pair of pliers or hard crushing object to crimp the end of the blue wire so that it compacts the coil.




**5** Do the same with the other blue wire and other end of the thermistor.




**6** If you have electrical tape, wrap some electrical tape around this joint.




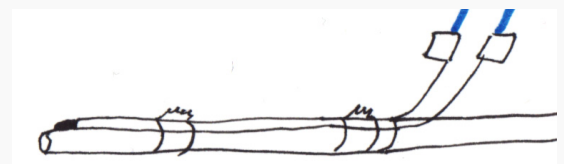**7** Finish off this step by taping your thermistor down onto the wooden dowel.



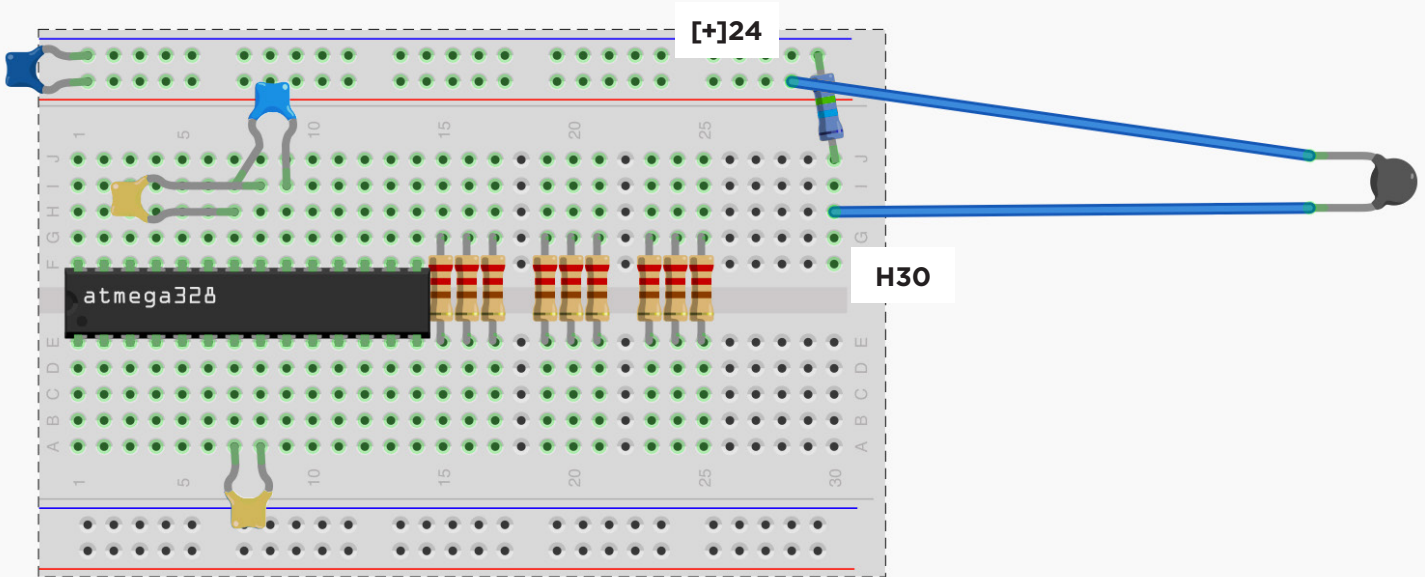

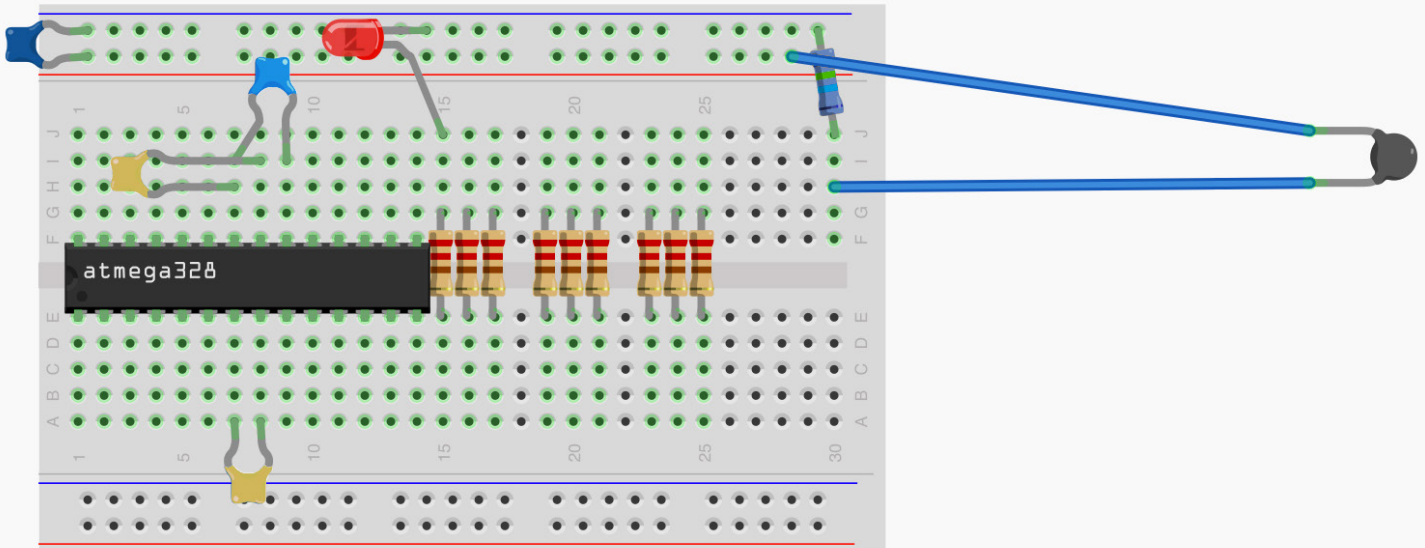The blue wires go in **[+24]** and **H30**.




Time to put in your LEDs.

LEDs have a long leg (anode) and a short leg (cathode).

Put the first of nine resistors on the breadboard:

Long leg in **J15**,

Short leg in **[-]12**.

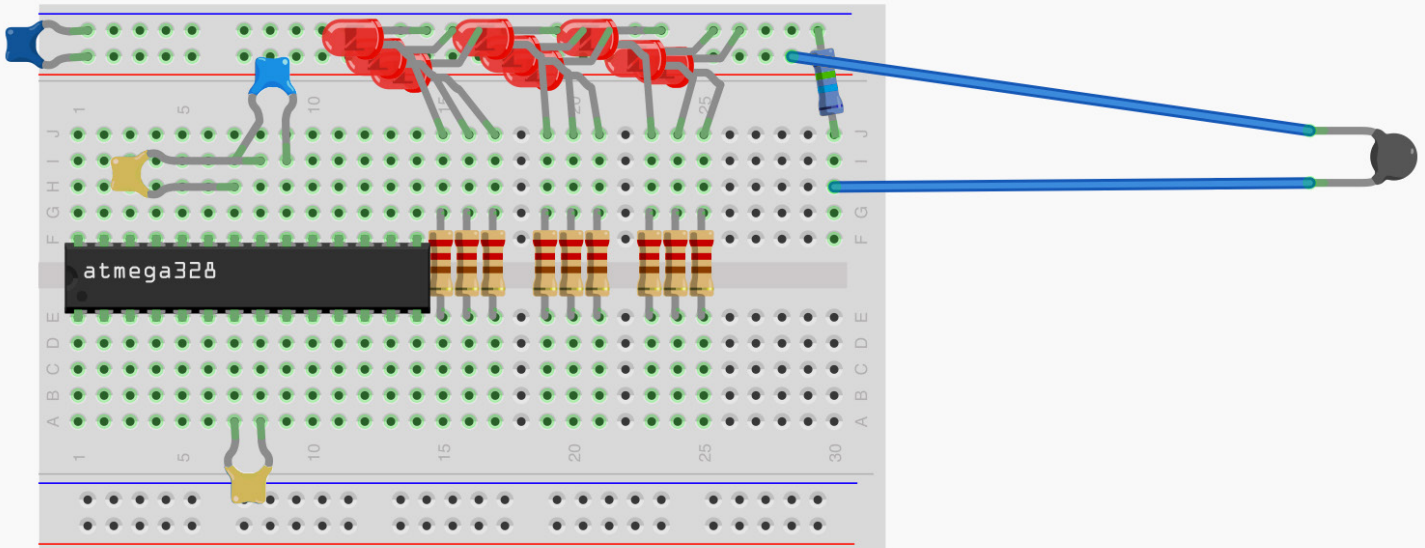

The rest of the LEDs goes on the board like this:

Long leg

Short leg

**J15** (just did)

**[-]12** (just did)

**J16**

**[-]13**

**J17**

**[-]14**

**J19**

**[-]16**

**J20**

**[-]17**

**J21**

**[-]18**

**J23**

**[-]20**


**J24**

**[-]21**

**J25**

**[-]22**



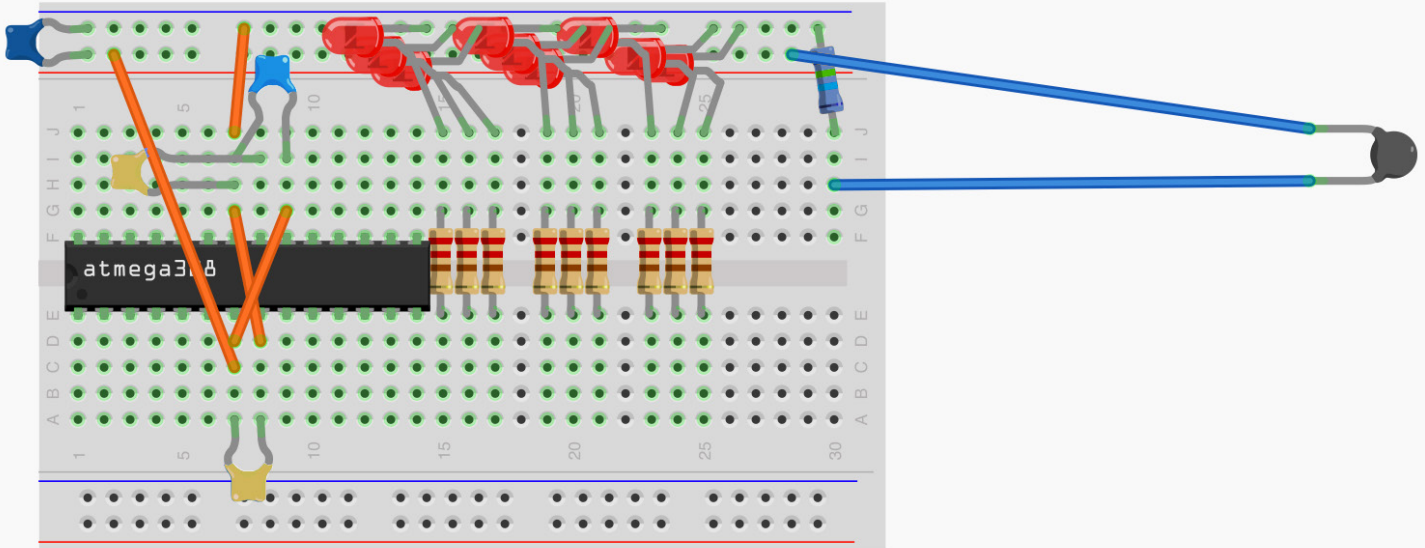

Put in your 3" orange wires:


**[+]2 to C7**

**[-]6 to J7**

**G7 to D8**

**G9 to D7**



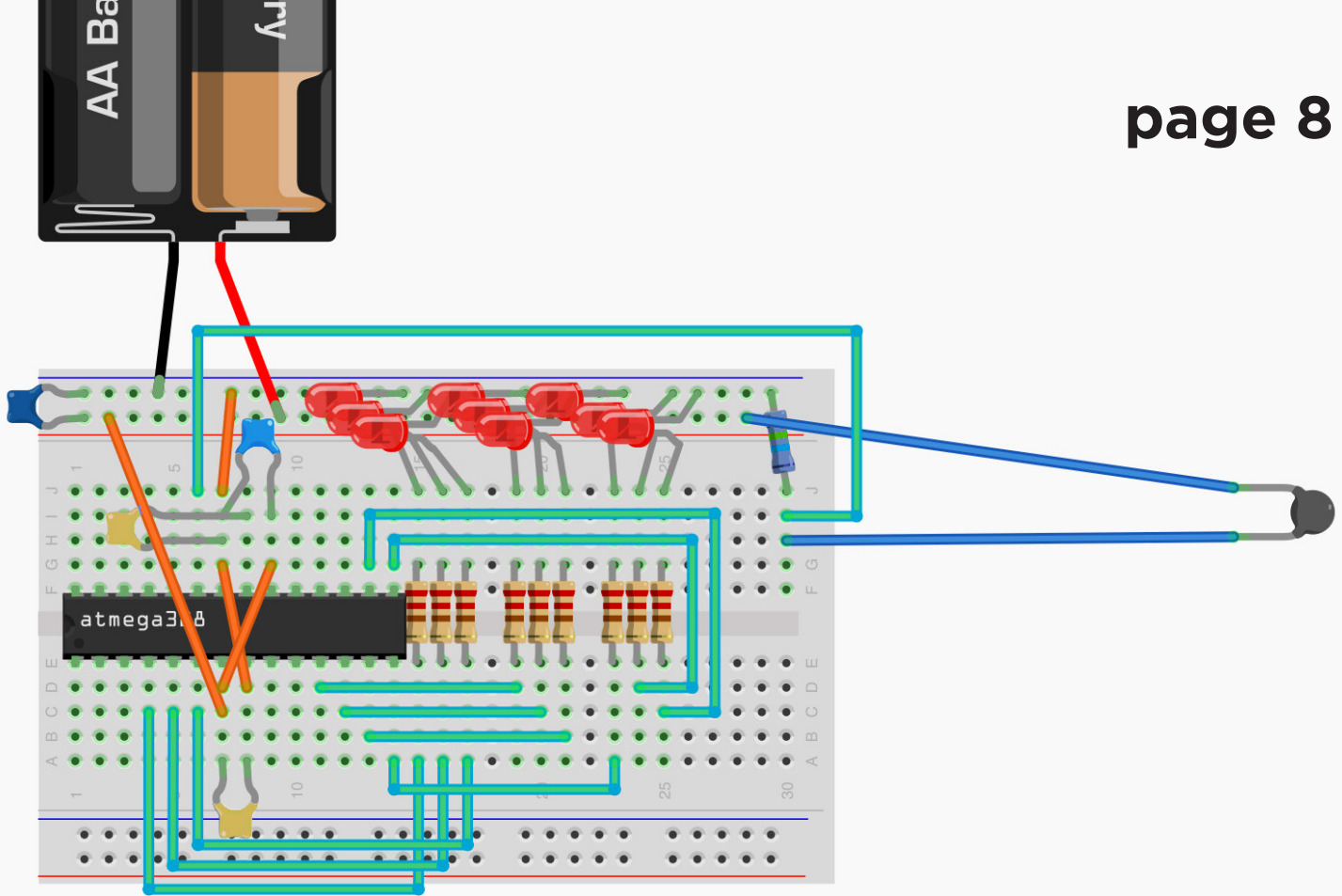

Connect your 5" green wires:

**J6 to i30**

**G13 to C25**

**G14 to D24**

**D11 to D19**

**C12 to C20**

**B13 to B21**

**A14 to A23**

**C4 to A15**

**C5 to A16**

**C6 to A17**

Battery wires go to **[-]4** and **[+]8**.

### Troubleshooting:

To test your finished tracker, take one leg of the thermistor out. Within 5 seconds the LEDs should light up.

If they don't, check the connection of your wires and LEDs.

Check the LEDs against the pattern at [wnyc.org/bugs](http://wnyc.org/bugs) to be sure all the LEDs are working.